

The drawing shows how to connect a pair of ADS8344 ADCs powered from 5V so as not to interfere with other QSPI peripherals and with the CF2's internal SPI connected supervisor. The 74ALVC1G125 are available from TI in SOT23-5 packages.

